
## My name is Mike Gentile. (yai can call me "Mike") Mgentile Ophysics. rutgers. edu Physics 194 - Lecture 7 Me (

Have a question during class? Please ask it right away, even if it means interrupting in the middle of a thought. I want you to!
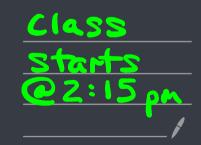
## Agenda

- Mathematical analysis of simple circuits
- Power
- Intro to the magnetic interaction




What you learned from using a voltmeter to analyze a circult -- Resister E = 9V E = 9V E = 4V RA battery's EMF (electronative Force) 18 has "strang" the  $\frac{R_{3}}{R_{0}} = \frac{R_{2}}{R_{0}}$ battery is. More or (ess have much every it gues each charge that  $\Delta V$ passes through it.  $|) \Delta V_{\mathcal{E}} + \Delta V_{\mathcal{R}_1} + \Delta V_{\mathcal{R}_2} + \Delta V_{\mathcal{R}_3} = 0$ Potential di Herence Kirchhoff (+) (-) (-) between 2 loop rule. points in  $\sum \Delta V = 0$ He circuit.

Har do you represent a battery mathematically?  $\Delta V_{c} = \epsilon$ a resistur device? what about How does BUR depend on I through it? L. M.A.  $\Delta \bigcup_{e} =$ that will vary ع ا - Vary DUR. DUE + DUR = O  $I = \frac{1}{R} \Delta V_R$ Ohm's (aw

 $\Delta V_R = \sum R (V|_A = R, the "ohn")$ (A) E = 120 V (v)


100,0

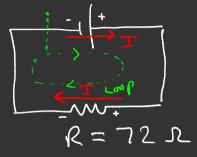


Power  $(A) (V) = T \Delta V$ (w = J(s))

 $\sum \Delta V = O$  $\Delta V_{g} + \Delta V_{R} = 0$  $+\epsilon - TR = 0$  $T = \frac{\varepsilon}{R} = \frac{120V}{72R} = 1.67 \text{ A}$  $P_{R} = I_{R} = (1.67A)(1200)$ = 200 W

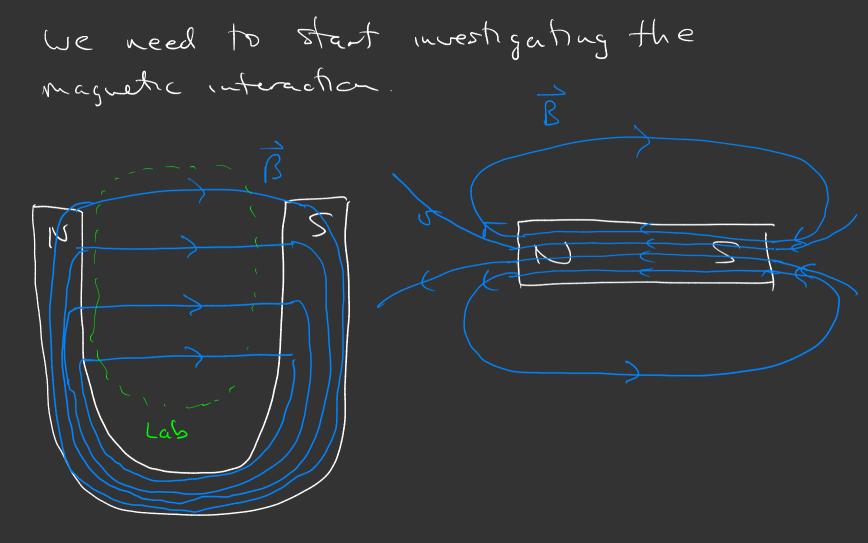Findamentally, a moring charged object produces a magnetic field!



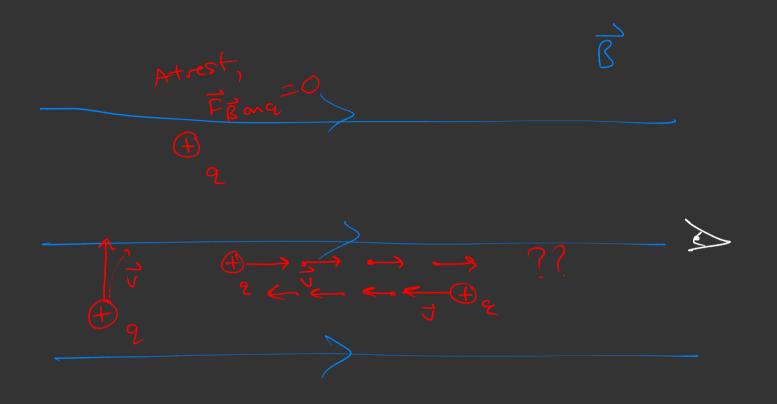

Right hand mile

